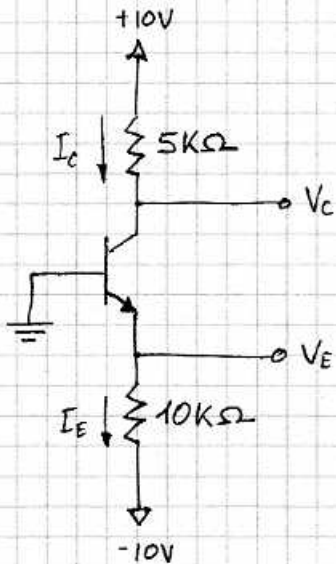


P205 es 4.8



$$V_E = -0,7V$$

$$\beta = 50$$

$$I_E = ?$$

$$I_B = ?$$

$$I_C = ?$$

$$V_C = ?$$

$$V_E = -V_{BE} \rightarrow V_{BE} = 0,7V$$

$$I_E = \frac{V_E - (-10)}{10k\Omega} = 0,93 \text{ mA}$$


$$\beta = 50 \rightarrow \alpha = \beta / (\beta + 1) = 0,9803$$

$$I_E = I_C / \alpha \rightarrow I_C = \alpha I_E = 0,912 \text{ mA}$$

$$I_B = I_C / \beta = 18,23 \mu A$$

$$(10 - V_C) = 5k\Omega \cdot I_C \rightarrow V_C = -(5 \cdot 10^3 \cdot 0,912 \cdot 10^{-3}) + 10 = 5,44 V$$

P205 es 4.9

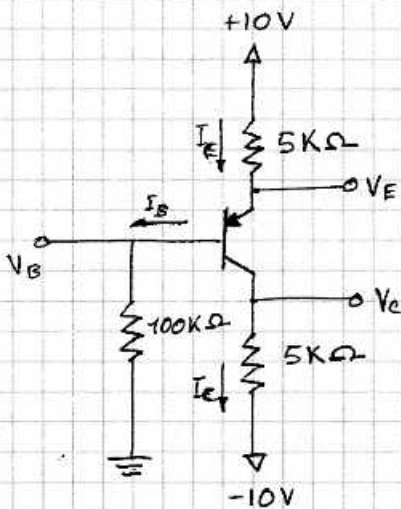

$$V_B = 1,0V$$

$$V_E = 1,7V$$

$$\alpha = ?$$

$$\beta = ?$$

$$V_C = ?$$

$$V_{EB} = V_E - V_B = 0,7V$$

$$I_E = \frac{10 - V_E}{5k\Omega} = 1,66 \text{ mA}$$

$$I_B = \frac{V_B}{100\text{K}\Omega} = 10\mu\text{A}$$

$$I_C = I_E - I_B = 1,65\text{mA}$$

$$I_B = I_C / \beta \rightarrow \beta = \frac{I_C}{I_B} = 165$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{165}{166} = 0,994$$

$$(V_C + 10) = 5\text{K}\Omega \cdot I_C \rightarrow V_C = (5\text{K}\Omega \cdot I_C) - 10 = -1,75\text{V}$$

P209 es. 4.11

$$V_A = 100\text{V}$$

$$I_{C1} = 0,1\text{mA} \quad Y_{01} = ?$$

$$I_{C2} = 1\text{mA} \quad Y_{02} = ?$$


$$I_{C3} = 10\text{mA} \quad Y_{03} = ?$$

$$Y_{01} = \frac{V_A}{I_{C1}} = 1\text{M}\Omega$$

$$Y_{02} = \frac{V_A}{I_{C2}} = 100\text{K}\Omega$$

$$Y_{03} = \frac{V_A}{I_{C3}} = 10\text{K}\Omega$$

P213 es 4.14

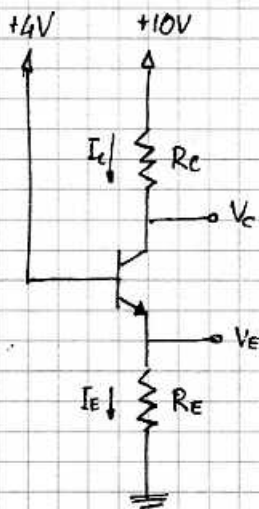

$$I_C = 0,5\text{mA}$$

$$V_{CE} = 2\text{V}$$

$$\alpha \approx 1$$

$$R_E = ?$$

$$R_C = ?$$

$$I_E = I_C / \alpha = 0,501 \text{ mA}$$


$$V_E = V_{CB} + V_B = 6 \text{ V}$$

$$R_E = \frac{(10 - V_E)}{I_C} = 8 \text{ k}\Omega$$

$$V_E = V_B - V_{BE} = 3,3 \text{ V}$$

$$R_E = \frac{V_E}{I_E} = 6,6 \text{ k}\Omega$$

P 214 es: 4.16

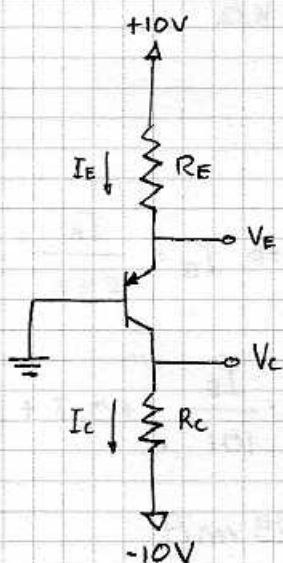

$$I_C = 1 \text{ mA}$$

$$V_{CB} = 4 \text{ V}$$


$$\alpha \approx 1$$

$$V_{EB} = 0,7 \text{ V}$$

$$I_E = \frac{(10 - 0,7)}{R_E} = \alpha I_C \rightarrow R_E = \frac{(10 - 0,7)}{\alpha I_C} = 9,3 \text{ k}\Omega$$

$$I_C = \frac{(4 - (-10))}{R_C} \rightarrow R_C = \frac{(4 - (-10))}{I_C} = 6 \text{ k}\Omega$$

P 214 esempio 4.6

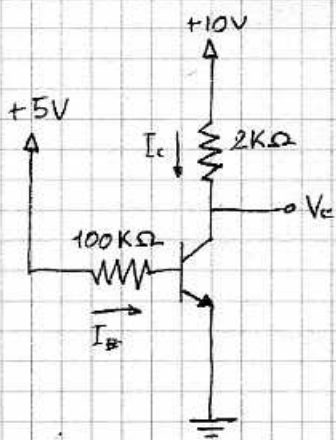

$$\beta = 100$$

$$I_B = \frac{5 - V_{BE}}{100 \text{ k}\Omega} = 43 \mu\text{A}$$

$$I_C = \beta \cdot I_B = 4,3 \text{ mA}$$

$$I_E = I_B + I_C = 4,343 \text{ mA}$$

$$V_C = 10 - (2 \text{ k}\Omega \cdot I_C) = 1,4 \text{ V}$$

